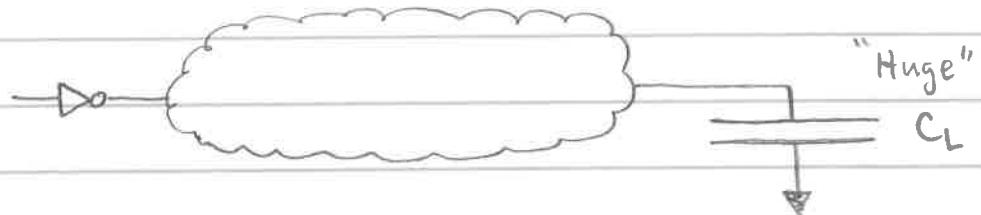


"Chain of Inverters" problem:

What circuit will drive a large load with the smallest delay?



First, some background:

C_g = input gate capacitance

C_{int} = intrinsic output capacitance (mostly diffusion cap.)

C_{ext} = cap. external to inverter (wire + load)

$$C_{int} = \gamma C_g \quad \text{"gamma"}$$

$\gamma \approx 1$ for modern processes, and is a function of technology


$$\begin{aligned} f &= \text{"effective fanout"} \\ &= C_{ext}/C_g \end{aligned}$$

$$t_p = t_{p_0} + t_{p_0} \frac{f}{\gamma}$$

= function of f only! [Key point]

$$\frac{f}{\gamma} = \frac{C_{ext}/C_g}{C_{int}/C_g} = \frac{C_{ext}}{C_{int}}$$

Back to chain of inverters:

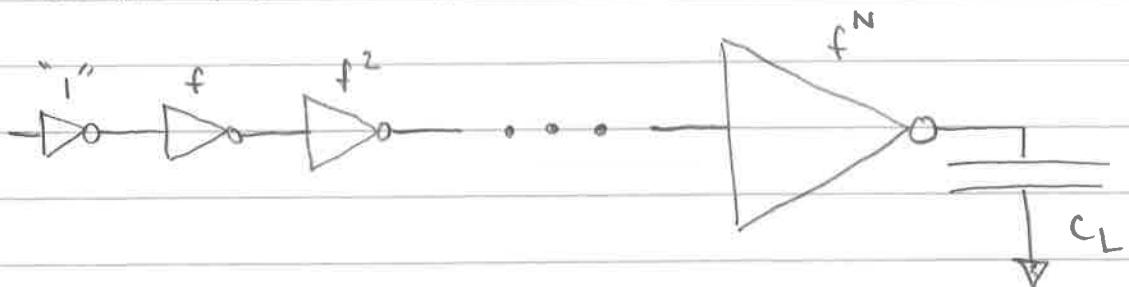

N = Number of stages

F = overall effective fanout

$$= C_L / C_{g_1}$$

C_{g_1} = C_g of first inverter

$$f = \sqrt[N]{F} \quad \text{for a constant } f \text{ across all stages}$$

Choose number of stages (N) to minimize delay for a given F

$$f = e^{(1+\gamma/F)}$$

1) Assume $\gamma = 0 \rightarrow C_{int} = 0$ simplification

$$N = \ln(F) \quad \text{solved closed form}$$

$$f = e$$

$$= 2.72$$


2) $\gamma = 1$ (more realistic)

$$f = 3.6 \quad \text{solved numerically}$$

book graph

Optimum $f \approx 3.6$. When that isn't possible, it is better to aim a little high rather than low.

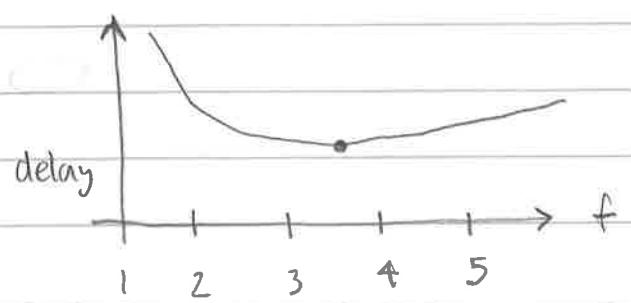- too low is very slow
- lower $f \rightarrow$ more gates




Ex: $F = 50$, neglect inversions, first inv has $W_p = 6x$, $W_n = 4x$

$$N=2 : \sqrt[2]{50} \approx 7$$

$$N=3 : \sqrt[3]{50} \approx 3.8 \quad \checkmark$$


$$N=4 : \sqrt[4]{50} \approx 2.8$$

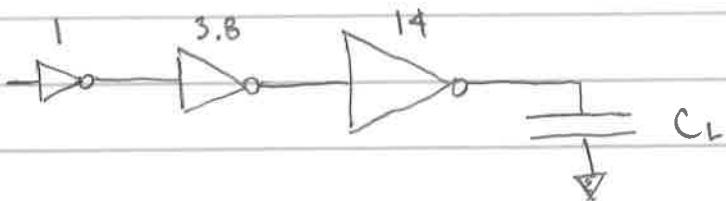



W_{PMOS}	6x	23x	84x
W_{NMOS}	4x	15x	56x

Of course if inversions are not negligible, we can choose only odd/even N value. Or:

a) Use \bar{Q} FF output instead of Q:

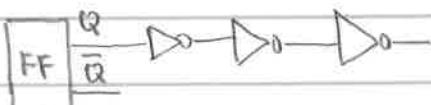

b) DFF input too

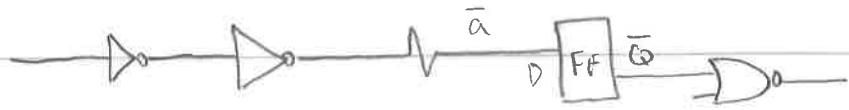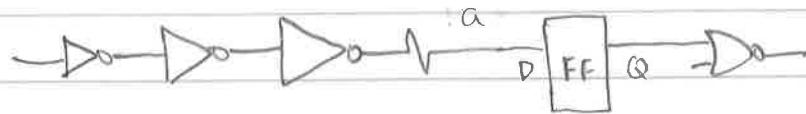

c) absorb into logic

