
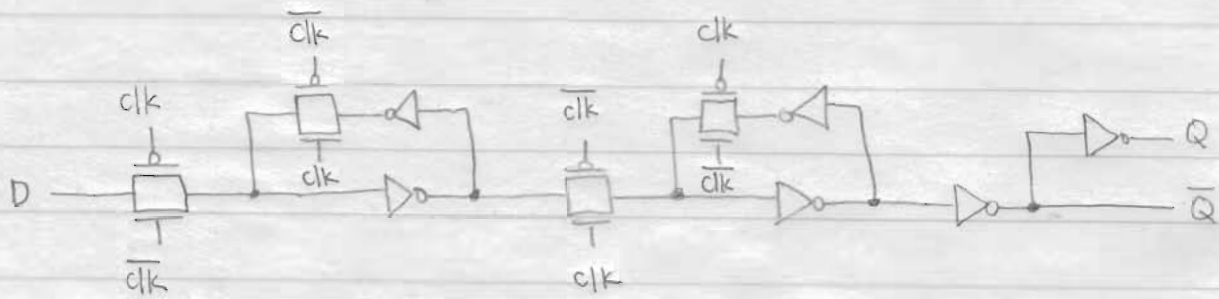


Safe Flip-Flop:

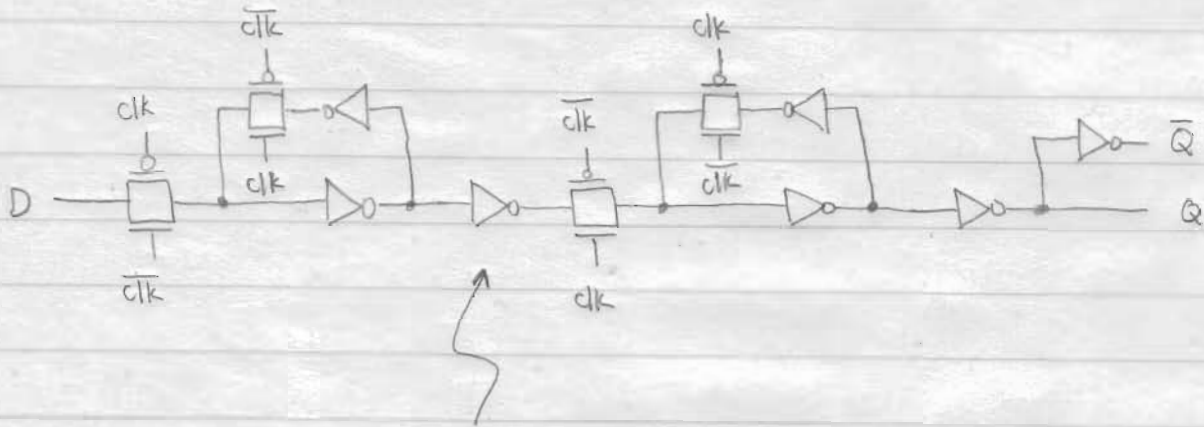

"Safest" Flip-Flop:



Inverter prevents feedback
back into first half of FF.