 



Layout Guidelines

① Orientation of Vdd/Gnd lines in schematics




③ Orientation of transistors

* transistors "vertical"
+ short poly

 



transistors "horizontal"

 - limited room to
stack transistors
+ easier to make wide transistors




② Stacking transistors

Ex:

  

Much better to "share diffusion"!

- smaller area

 


④ Routing of VDD/Gnd

- in metal (poly probably never, diff. only for short distances)

* - metal 1


+ very convenient

• most common

 

- metal 2

 
+ signals can easily go under power/ground



• Use wider wires (67 for bus), large (many) contacts

⑤ <see p. 2.1>

⑥ Cell placement

 


- Vdd/Gnd wires line up

← row skipped, check Vdd/Gnd wire

⑦ Metal routing discipline

 Suppose we want to route across this cell vertically




must go to metal 5!

Key point: every wire blocks perpendicular wires from using that layer

⑤ Rows of diffusion in a cell

* Two:

- preferable

 

Four:



- often has large

empty spaces

+ easier for more complex cells

- harder to use with std.-height cells


• generally avoid if possible

  

a) Guideline: Try to use only m1 and m2 in small cells

b) Guideline: Use only one direction for each layer.


Ex: (bad)

 

c) Guideline: Alternate directions for each layer

EX: horizontal = m1, m3, m5


vertical = m2, m4, m6

 


② Stack vias: to reduce area

In old days, this was not possible

EX: m1 to m3

 

Now thanks to CMP, they can be stacked

 

Remember m2 is blocked!

Most ^{advanced} processes can stack arbitrarily high

but in Magic: pm12c

m123c

m234c

m345c


m456c

(pdm12c (pdiff, m1, m2)
(ndm12c (ndiff, m1, m2))


9) Reduce area

a) share, overlap (Ex: Vdd and Gnd)


Ex: parallel wires

 

Ex: 2 inverters

 


better:

 

b) Abut




better:

 


c) Avoid wires that turn corners, if possible


ii.)

 

i.)

 

* iii.)

 


"pitch matching"



pitch of A cells matched with pitch of B cells

d) Consider shape of overall structure


Ex: 32-bit adder

 

  
• For an arbitrary block, a square shape will give the shortest total wire length



 e) Transistor folding (for large devices)



 - large source & drain caps.
- with very wide trans., will not fit inside the allotted cell height



- source cap is larger (good)
- drain cap is reduced (good)

⑩ Reduce max. delay

$$t_p = 0.69 R_{mos} C_L$$

- Reduce R_{mos}

• In layout, means wider transistors

but this increases load cap. for driving gate

helps a lot for under-driven nets, diminishing returns eventually

- Reduce C_L

• shorter wires \leftrightarrow smaller area $\xrightarrow{\hspace{2cm}}$ lower $C_L \rightarrow$ reduce mos widths
 \rightarrow smaller area ...

• use higher-level metals if possible

⑪ Reduce power

$$P = C_L V^2 f$$

* Reduce C_L

V_{dd} and f generally set by other requirements

Other more complex techniques possible