

# BINARY MULTIPLICATION

# Multipliers

---

- Multipliers are widely used in digital signal processing, generally more so than in general-purpose workloads
- Major categories of multiplier types
  - *Unsigned × Unsigned*  
Also very useful for sign-magnitude data
  - *Signed 2's complement × Signed 2's complement*  
Very useful for fixed-point 2's complement data
- Hardware is typically built in a manner broadly similar to how you would do it with paper and pencil
- The naming convention is somewhat unfortunate:

*multipl*  
*x*      *multiplier*

---

# Multipliers

- Example: 4-bit unsigned *multiplicand* “ $a$ ” times 4-bit *multiplier* “ $b$ ”
- $b$  could be signed or unsigned
- $p_{xy} = a_x \times b_y$   
 $= a_x \text{ AND } b_y$

		$a_3$	$a_2$	$a_1$	$a_0$			
	×	$b_3$	$b_2$	$b_1$	$b_0$			
		$p_{30}$	$p_{20}$	$p_{10}$	$p_{00}$	← $b_0$		
		$p_{31}$	$p_{21}$	$p_{11}$	$p_{01}$	0	← $b_1$	
	$p_{32}$	$p_{22}$	$p_{12}$	$p_{02}$	0	0	← $b_2$	
	$p_{33}$	$p_{23}$	$p_{13}$	$p_{03}$	0	0	0	← $b_3$

# Multipliers

- Example: 4-bit signed 2's complement *multiplicand* "a" times 4-bit *multiplier* "b"
- b could be signed or unsigned


- s = partial product sign extension bits

- $p_{xy} = a_x \times b_y$   
=  $a_x$  AND  $b_y$

				$a_3$	$a_2$	$a_1$	$a_0$	
			×	$b_3$	$b_2$	$b_1$	$b_0$	
$s$	$s$	$s$	$s$	$p_{30}$	$p_{20}$	$p_{10}$	$p_{00}$	$\leftarrow b_0$
$s$	$s$	$s$	$p_{31}$	$p_{21}$	$p_{11}$	$p_{01}$	0	$\leftarrow b_1$
$s$	$s$	$p_{32}$	$p_{22}$	$p_{12}$	$p_{02}$	0	0	$\leftarrow b_2$
$s$	$\overline{p_{33}}$	$\overline{p_{23}}$	$\overline{p_{13}}$	$\overline{p_{03}}$	0	0	0	$\leftarrow b_3$

# 3 Main Steps in Every Multiplier

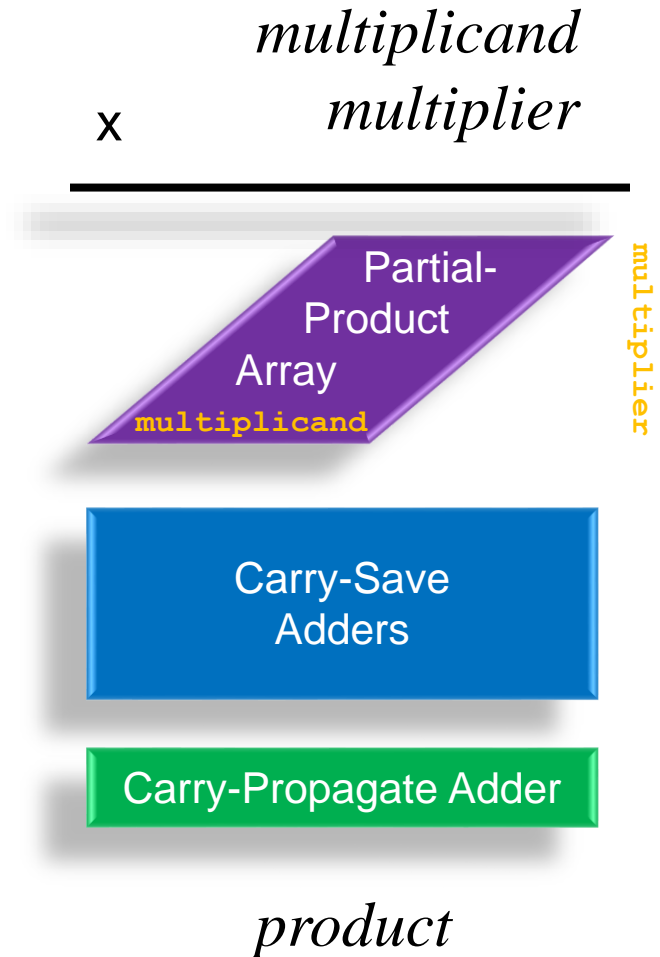
- 1) Generation of partial products
- 2) Reduction or “compression” of the partial product array (normally using carry-save addition) so that the product is composed of two words
  - Linear array addition
  - Tree addition (Wallace tree)
- 3) Final adder: Carry-propagate adder (CPA)
  - Converts the product in carry-save form into a single word form
  - Any style of CPA is fine though we probably favor faster ones



# Straight-forward Partial Product Generation

- This is the simplest method to generate partial products
- Hardware looks at one bit of the *multiplier* ( $Y_i$ ) at a time
- Partial products are copies of the *multiplicand* AND'd by bits of the *multiplier*
- Number of bits in the *multiplier*  
= Number of partial products  
= Number of terms/words/rows that must be added

$Y_i$	Partial product
0	0
1	$+x (= \textit{multiplicand})$

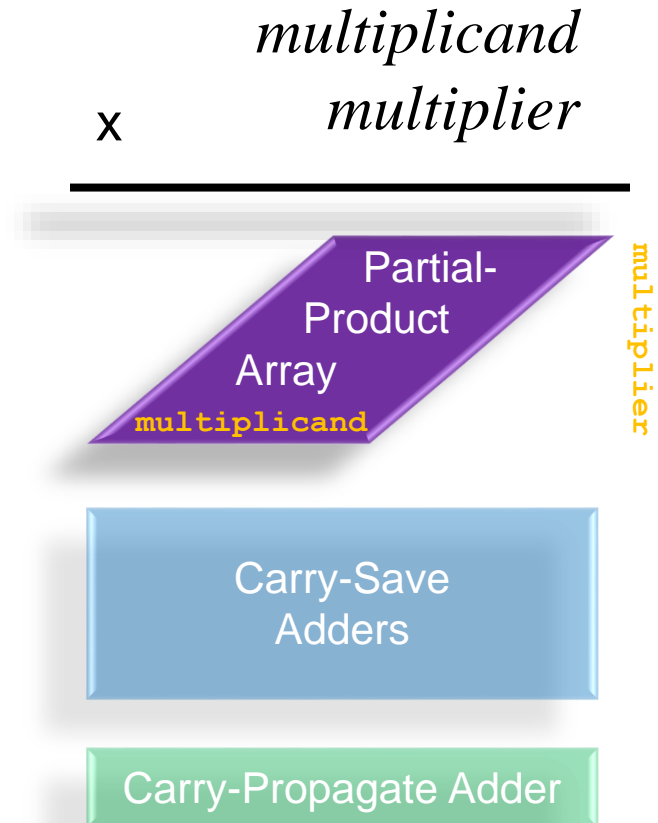

# Straight-forward Partial Product Generation

- There are only two possible partial product results
- Two reasonable hardware solutions are:
  - a row of 2:1 muxes with zeros on one input
  - a row of AND gates (this should be more efficient)

+x

*multiplicand*

0

0

$Y_i$	Partial product
0	0
1	+x (= <i>multiplicand</i> )





# Example 2's complement 4-bit × 4-bit multiplication

- Example: 4-bit signed 2's complement *multiplicand* "a" 1100 times 4-bit *multiplier* "b" 1010
- $1100 \times 1011 = -4 \times -5 = +20$
- $1100 \times 1011 = (-4 \times -8) + (-4 \times 0) + (-4 \times 2) + (-4 \times 1) = +20$
- $00010100 = 16 + 4 = +20$  😊

				1	1	0	0	
				×	1	0	1	1
1	1	1	1	1	1	0	0	← 1
1	1	1	1	1	0	0	0	← 1
0	0	0	0	0	0	0	0	← 0
0	1	1	0	1	0	0	0	← 1
0	0	0	1	0	1	0	0	